

# EECS151/251A

## Introduction to Digital Design and ICs


### Lecture 23: SRAM II

Sophia Shao



Robert Dennard

 - Invented DRAM in 1968 at IBM
- Formulate Dennard's scaling: Maintain constant power density with improved frequency/performance
- The end of Dennard's scaling leads to the inability to further increase clock frequencies and multicore processors as an alternative way to improve processor performance




# Review

- Flip-flop is typically a latch pair
- Setup and hold times are defined at constant percentage increases over clk-q delay
- SRAM has unique combination of density, speed, power




- **SRAM**
  - 6-T SRAM Cell
  - Sizing SRAM Cell
- **Memory Decoder**
  - Overview
  - Decoder Design
  - Pre-decoder
- **Multi-Ported SRAM**

# SRAM Cell

 

# 6-transistor CMOS SRAM Cell

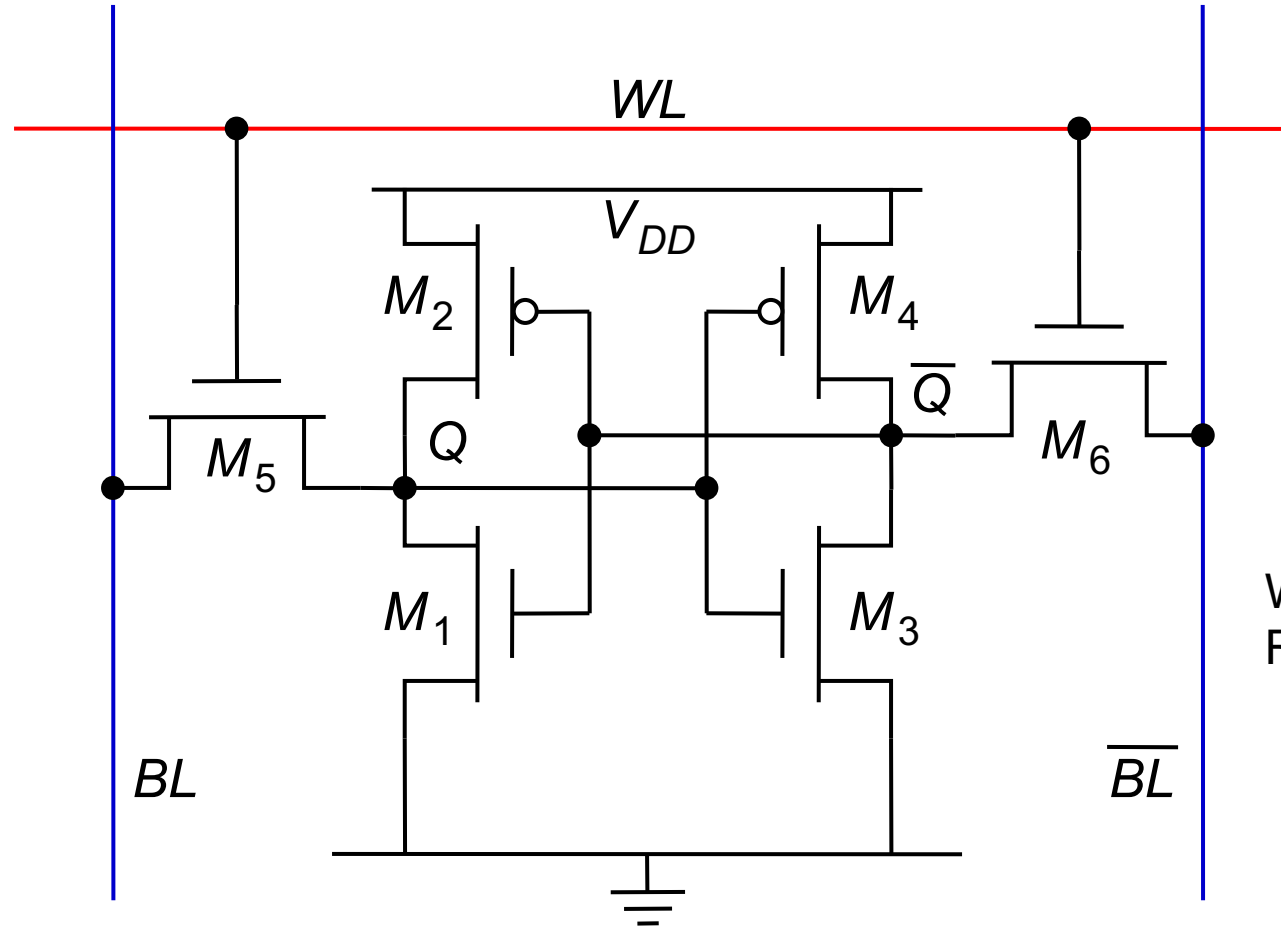


Write:  $BL$  and  $\bar{BL}$  are inverted.  
Read:  $BL$  and  $\bar{BL}$  are  $V_{DD}$

- Wordline ( $WL$ ) enables read/write access for a row
- Data is written/read differentially through shared  $BL$ ,  $\bar{BL}$

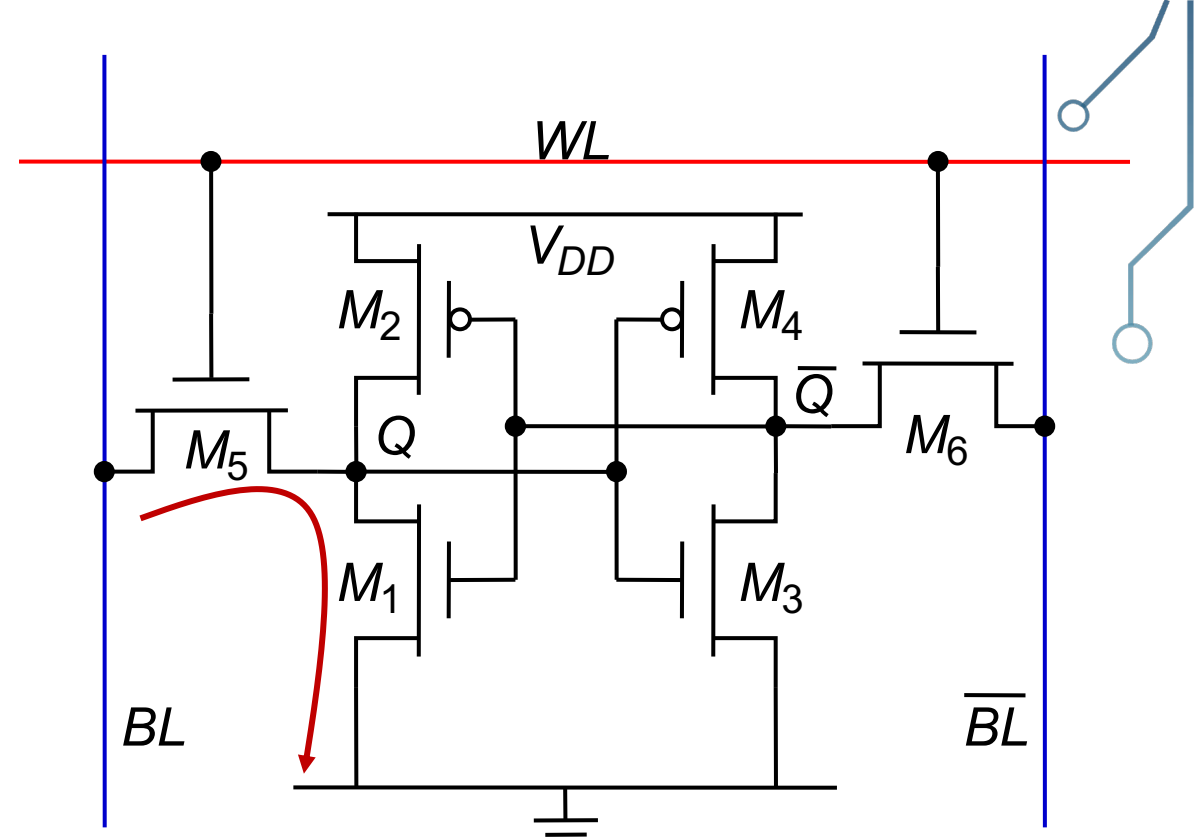
# Sizing SRAM Cell

- Read stability: Cell should not change value during read
  - $Q = 0$ :  $M_5$ ,  $M_1$  both on
  - Voltage divider between  $M_5$ ,  $M_1$
  - $V_Q$  should stay low, not to flip  $M_4$ - $M_3$  inverter
  - $R_1 < R_5 \Rightarrow (W/L)_1 > (W/L)_5$
- Typically  $(W/L)_1 = 1.5 (W/L)_5$ 
  - In FinFETs:  $(W/L)_1 = 2(W/L)_5$
- Read speed: Both  $M_5$  and  $M_1$


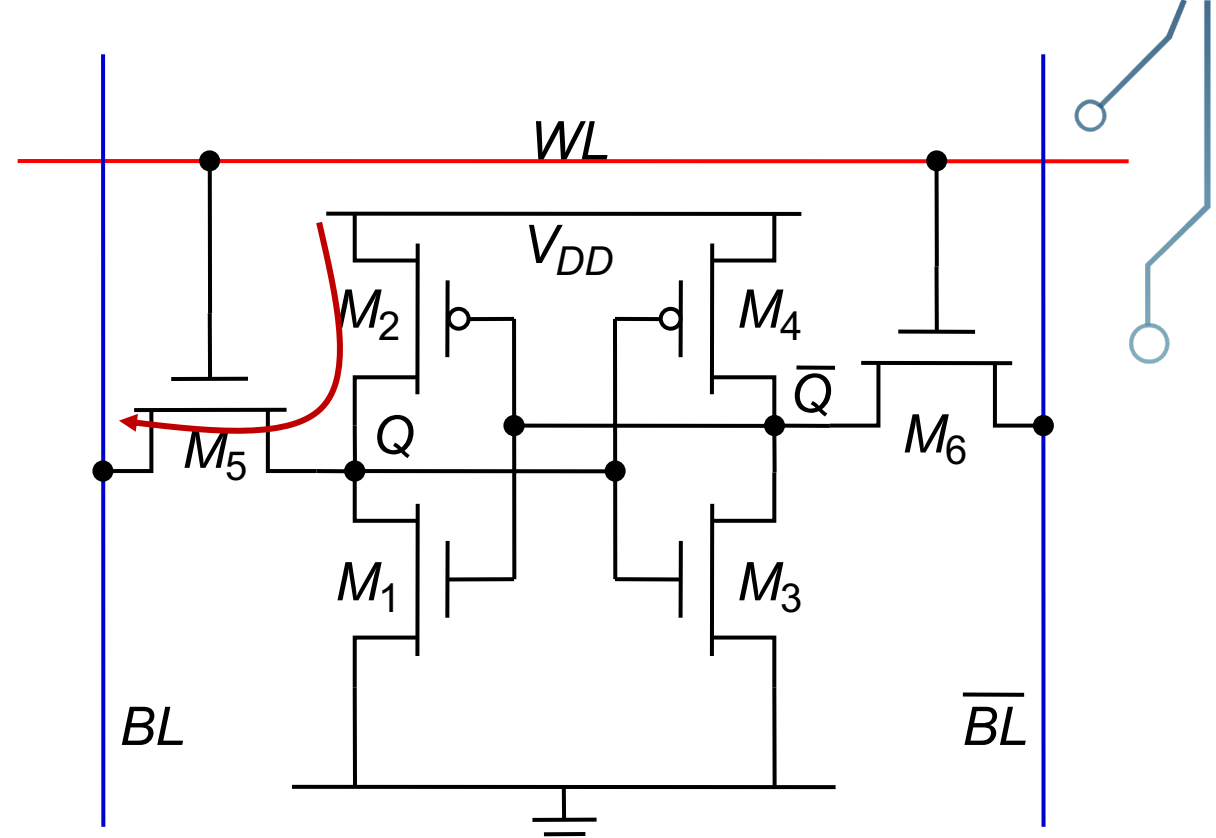
# Sizing SRAM Cell

- Writeability: Cell should be writeable by pulling BL low
  - $Q = 1$ ,  $M_5$ ,  $M_2$  both on
  - Voltage divider between  $M_5$ ,  $M_2$
  - $V_Q$  should pull below the switching point of  $M_4$ - $M_3$  inverter
  - $R_5 < R_2 \Rightarrow (W/L)_5 > (W/L)_2$
- Typically  $(W/L)_5 = (W/L)_2$  in planar
  - In FinFETs:  $(W/L)_5 = 2(W/L)_2$
  - Pull Up: Access: Pull Down:
    - 1:2:2 and 1:2:3 sizing



# True or False


1. Transistor leakage doesn't affect SRAM read speed.
2. One should write into an SRAM cell by pulling BL high.
3. One can write into a part of a selected WL.





- **SRAM**
  - 6-T SRAM Cell
  - Sizing SRAM Cell
- **Memory Decoder**
  - Overview
  - Decoder Design
  - Pre-decoder
- **Multi-Ported SRAM**

# Decoders

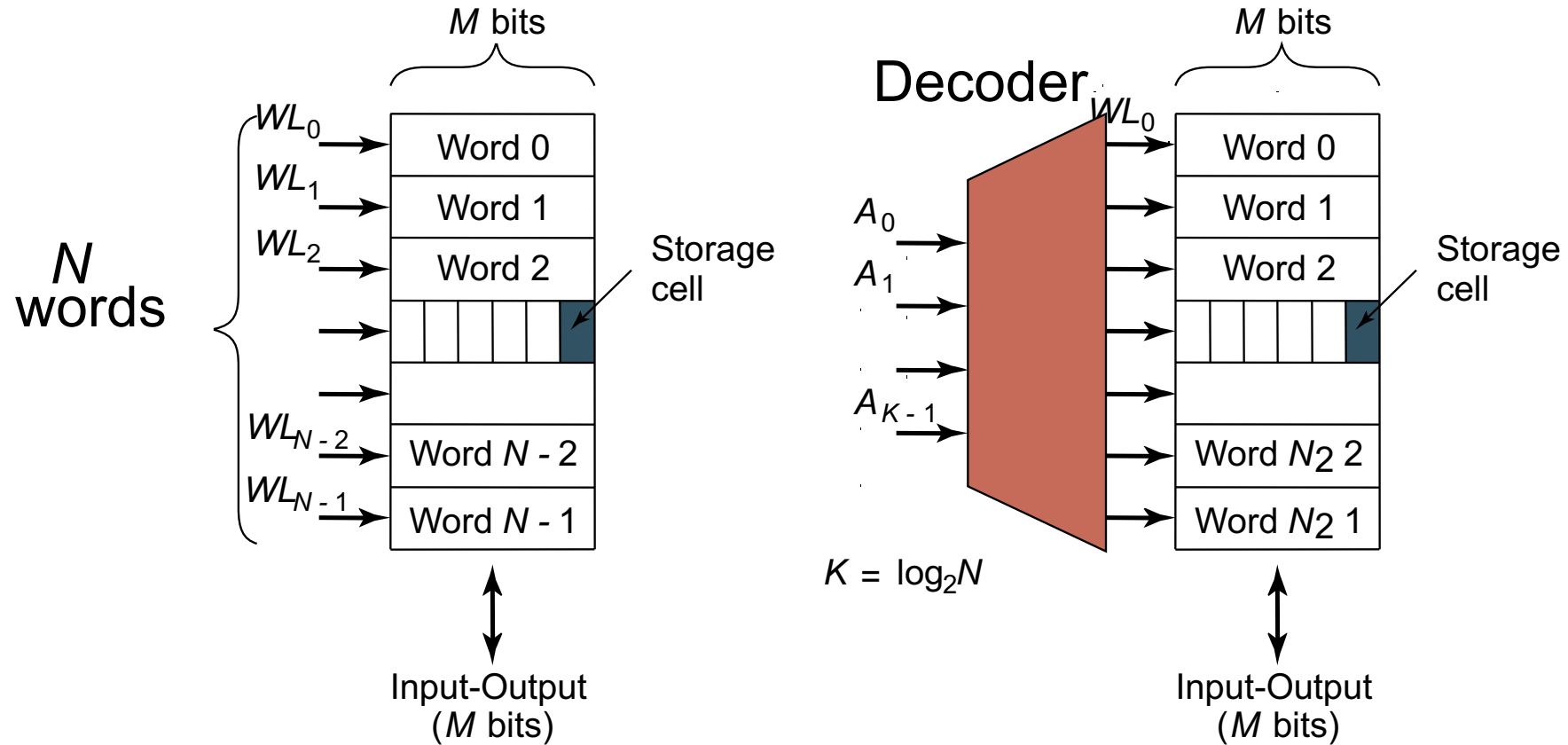

Intuitive architecture for  $N \times M$  memory

Too many select signals:

$N$  words =  $N$  select signals

Decoder reduces the number of select signals

$$K = \log_2 N$$

# Row Decoders

Collection of  $2^N$  complex logic gates  
Organized in regular and dense fashion

## (N)AND Decoder


$$WL_0 = \overline{A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9}$$

$$WL_{511} = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 \overline{A_9}$$
 
## NOR Decoder


$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{\overline{A_0} + \overline{A_1} + \overline{A_2} + \overline{A_3} + \overline{A_4} + \overline{A_5} + \overline{A_6} + \overline{A_7} + \overline{A_8} + A_9}$$



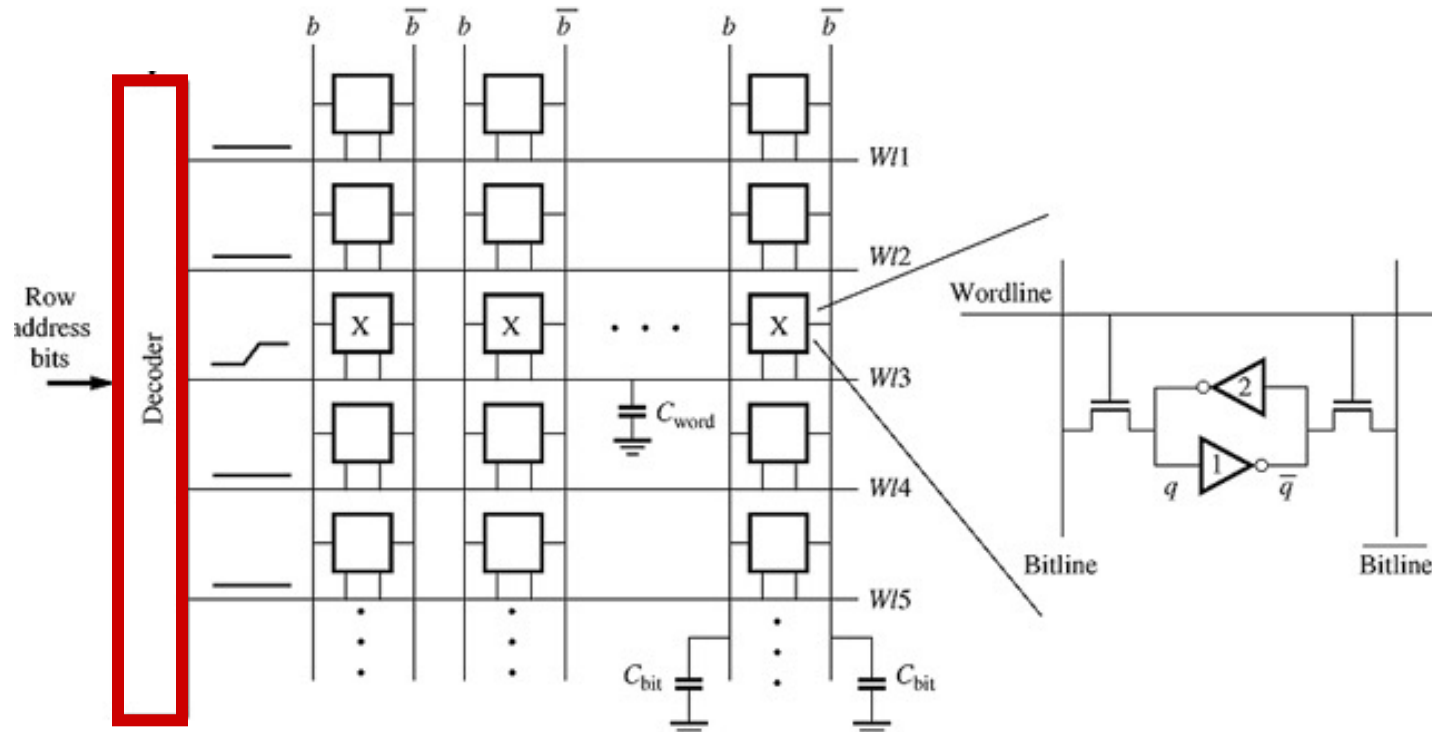
# Decoder Design Example

- Look at decoder for 256x256 memory block (8KBytes)



 
# Possible Decoder

- 256 8-input AND gates
  - Each built out of a tree of NAND gates and inverters
- Need to drive a lot of capacitance (SRAM cells)
  - What's the best way to do this?




# 8-Input AND

 

$LE : 9/2$	1	$LE : 5/2$	$3/2$	$LE : 3/2$	$3/2$	$3/2$	1
$\prod LE = 9/2$		$\prod LE = 15/4$		$\prod LE = 27/8$			
$P = 8 + 1$		$P = 4 + 2$		$P = 2 + 2 + 2 + 1$			

 
# 8-Input AND

- Using 2-input NAND gates
  - 8-input gate takes 6 stages
- Total LE is  $(3/2)^3 \approx 3.4$






 
# Decoder So Far

- 256 8-input AND gates
  - Each built out of tree of NAND gates and inverters
- Issue:
  - Every address line has to drive 128 gates (and wire) right away
  - Forces us to add buffers just to drive address inputs






# Look Inside Each AND8 Gate

    

# Predecoders


- Use a single gate for each of the shared terms
  - E.g., from  $A_0$ ,  $\overline{A_0}$ ,  $A_1$ , and  $\overline{A_1}$ , generate four signals:  $A_0A_1$ ,  $\overline{A_0}A_1$ ,  $A_0\overline{A_1}$ ,  $\overline{A_0}\overline{A_1}$
- In other words, we are decoding smaller groups of address bits first
  - And using the “predecoded” outputs to do the rest of the decoding

# Predecoder and Decoder

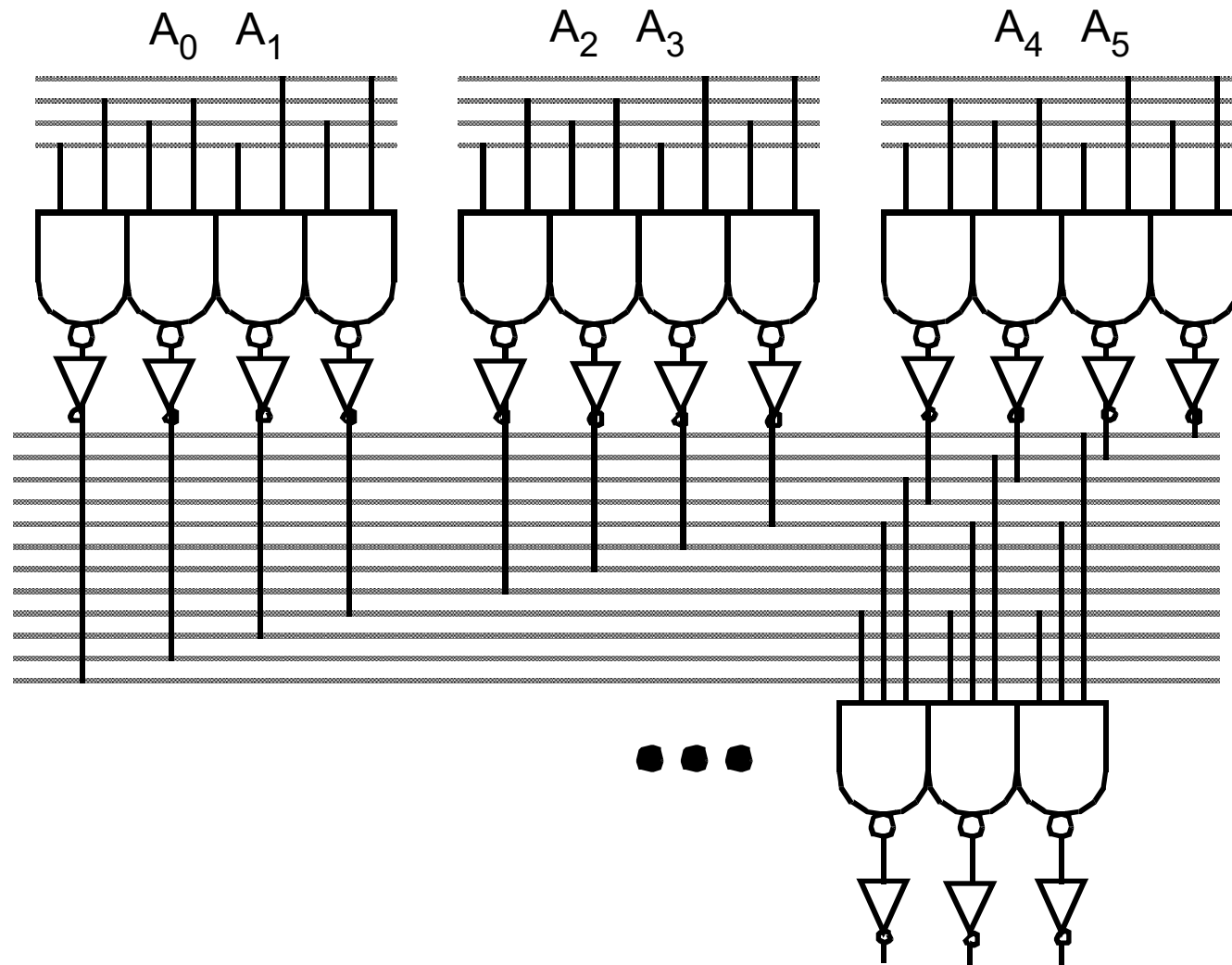
 
# Predecode Options

- Larger predecode usually better:
- More stages before the long wires
  - Decreases their effect on the circuit
- Fewer number of long wires switches
  - Lower power
- Easier to fit 2-input gate into cell pitch






- **SRAM**
  - 6-T SRAM Cell
  - Sizing SRAM Cell
- **Memory Decoder**
  - Overview
  - Decoder Design
  - Pre-decoder
- **Multi-Ported SRAM**

 
# Multi-Ported Memory

- Motivation:
  - Consider CPU core register file:
    - 1 read or write per cycle limits processor performance.
    - Complicates pipelining. Difficult for different instructions to simultaneously read or write regfile.
    - Single-issue pipelined CPUs usually needs 2 read ports and 1 write port (2R/1W).
    - Superscalar processors have more (e.g. 6R/3W)



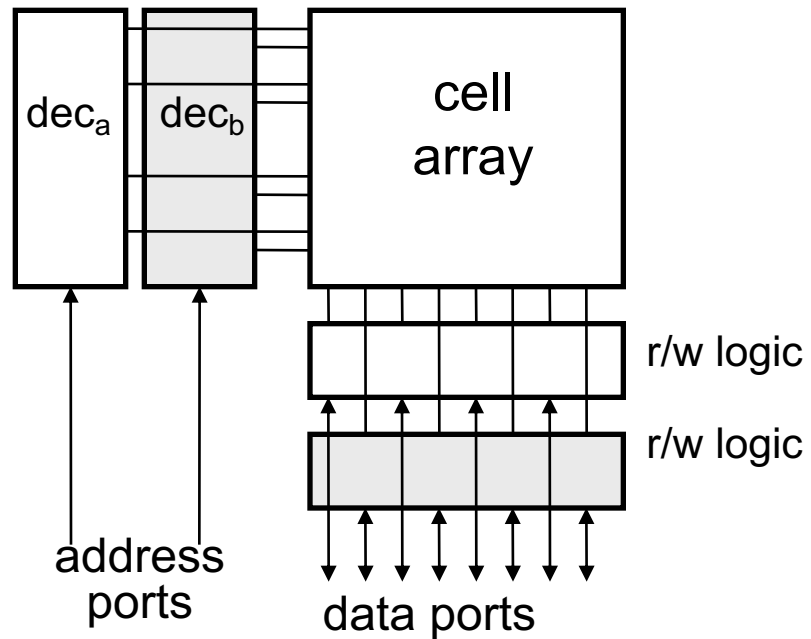
# Dual-Ported Memory Internals

- Add decoder, another set of read/write logic, bits lines, word lines:




- Example cell: SRAM

 

- Repeat everything but cross-coupled inverters.
- This scheme extends up to a couple more ports, then need to add additional transistors.

# 1R/1W 8T SRAM

8-T SRAM

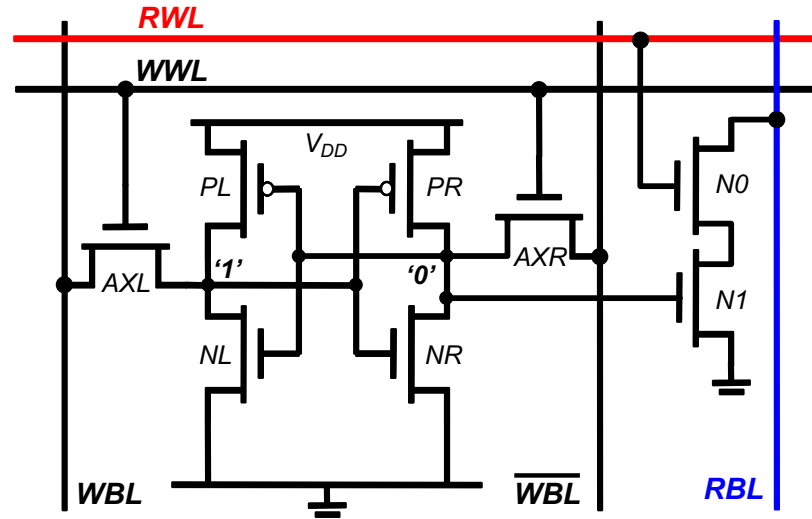

- Write:
  - $RWL = 0$
  - $WWL = 1$
- Read:
  - $WWL = 0$
  - $RWL = 1, RBL = V_{dd}$

- Dual-port read/write capability
- Single-cycle read and write, timed appropriately
- Often found in register files, first level (L1) of cache



# Summary

- SRAM cells sized for stability and writeability.
- Memory decoder & pre-decoder:
  - Decoder is a series of AND gates that drive word lines.
  - One decoder per read/write port.
  - Broken into predecoder for better area and delay.
- Multi-ported SRAM
  - Improve bandwidth requirement
  - Typically lead to duplicate resources like decoders, access transistors.