

# EECS151/251A

## Introduction to Digital Design and ICs

### Lecture 20: Multipliers

Sophia Shao




#### NVIDIA Announces Hopper Architecture, the Next Generation of Accelerated Computing

To power the next wave of AI data centers, NVIDIA today announced its next-generation accelerated computing platform with NVIDIA Hopper™ architecture, delivering an order of magnitude performance leap over its pre-

Named for Grace Hopper, a pioneering U.S. computer scientist, the new architecture succeeds the NVIDIA , architecture, launched two years ago.

The company also announced its first Hopper-based GPU, the NVIDIA H100, packed with 80 billion transistors. As the world's largest and most powerful accelerator, the H100 has groundbreaking features such as a revolutionary Transformer Engine and a highly scalable NVIDIA NVLink® interconnect for advancing gigantic AI language deep recommender systems, genomics and complex digital twins.
 
<https://nvidianews.nvidia.com/news/nvidia-announces-hopper-architecture-the-next-generation-of-accelerated-computing>



# Review

- Binary adders are a common building block of digital systems
- Carry is in the critical path
- Carry-bypass, carry-select are usually faster than ripple-carry for lengths  $> 8$
- Carry-lookahead,  $O(\sim \log N)$  is often the fastest adder with  $N > 16$



- **Multipliers**

- **Basics**
- **Parallel Multipliers**
- **Booth Recoding**
- **Signed Multipliers**

# Warmup

- Recall long multiplication of base-10 by hand:

$$\begin{array}{r} 12 \\ \times 56 \\ \hline \end{array}$$

- In base-2 (binary), we do the same thing:

$$\begin{array}{r} 011 \\ \times 101 \\ \hline \end{array}$$


# Multiplication

$$\begin{array}{rcccc}
 & a_3 & a_2 & a_1 & a_0 & \leftarrow \text{Multiplicand} \\
 \times & b_3 & b_2 & b_1 & b_0 & \leftarrow \text{Multiplier} \\
 \hline
 & & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 & & & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 & & & & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 \\
 & a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 & & & \\
 \hline
 & \dots & & a_1b_0 + a_0b_1 & a_0b_0 & \leftarrow \text{Product}
 \end{array}$$

} *Partial products*

Many different circuits exist for multiplication.  
 Each one has a different balance between *speed (performance)* and  
 amount of *logic (energy, cost)*.

# “Shift and Add” Multiplier

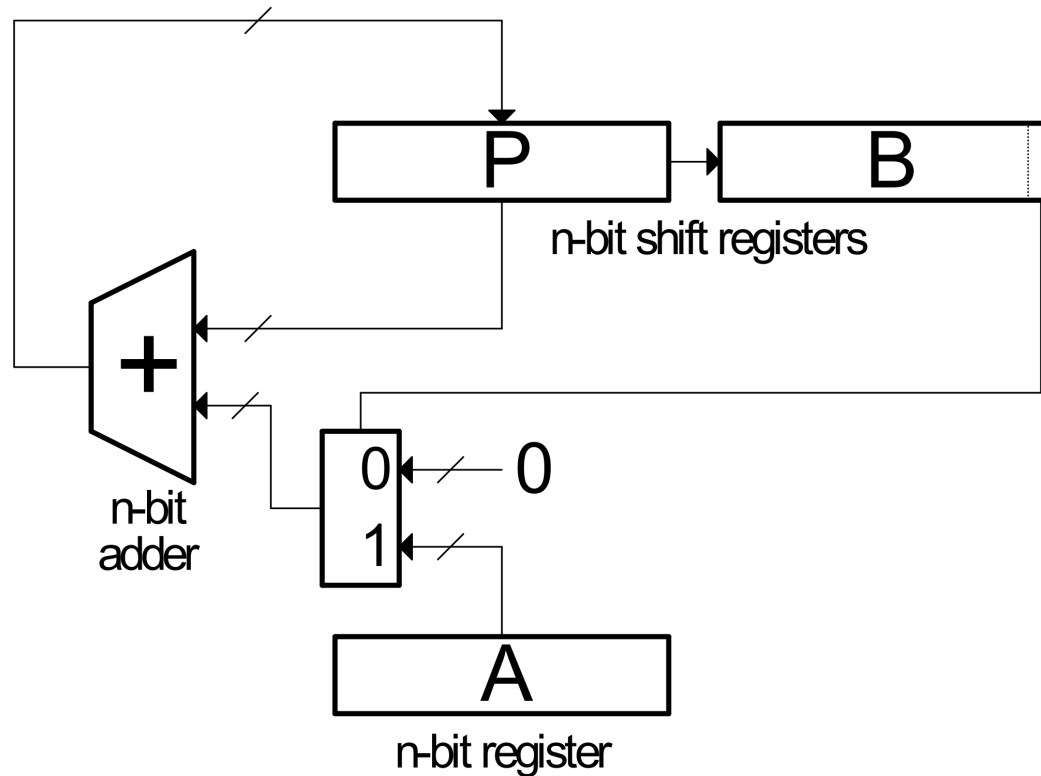

- Performance:  $N$  cycles of  $N$ -bit additions

- Sums each partial product, one at a time.
- In binary, each partial product is shifted versions of  $A$  or  $0$ .

Control Algorithm:

1.  $P \leftarrow 0$ ,  $A \leftarrow$  multiplicand,  $B \leftarrow$  multiplier
2. If LSB of  $B == 1$  then add  $A$  to  $P$   
else add  $0$
3. Shift  $[P][B]$  right 1
4. Repeat steps 2 and 3  $(n-1)$  more times.
5.  $[P][B]$  has product.



- **Multipliers**


- **Basics**
- **Parallel Multipliers**
- **Booth Recoding**
- **Signed Multipliers**


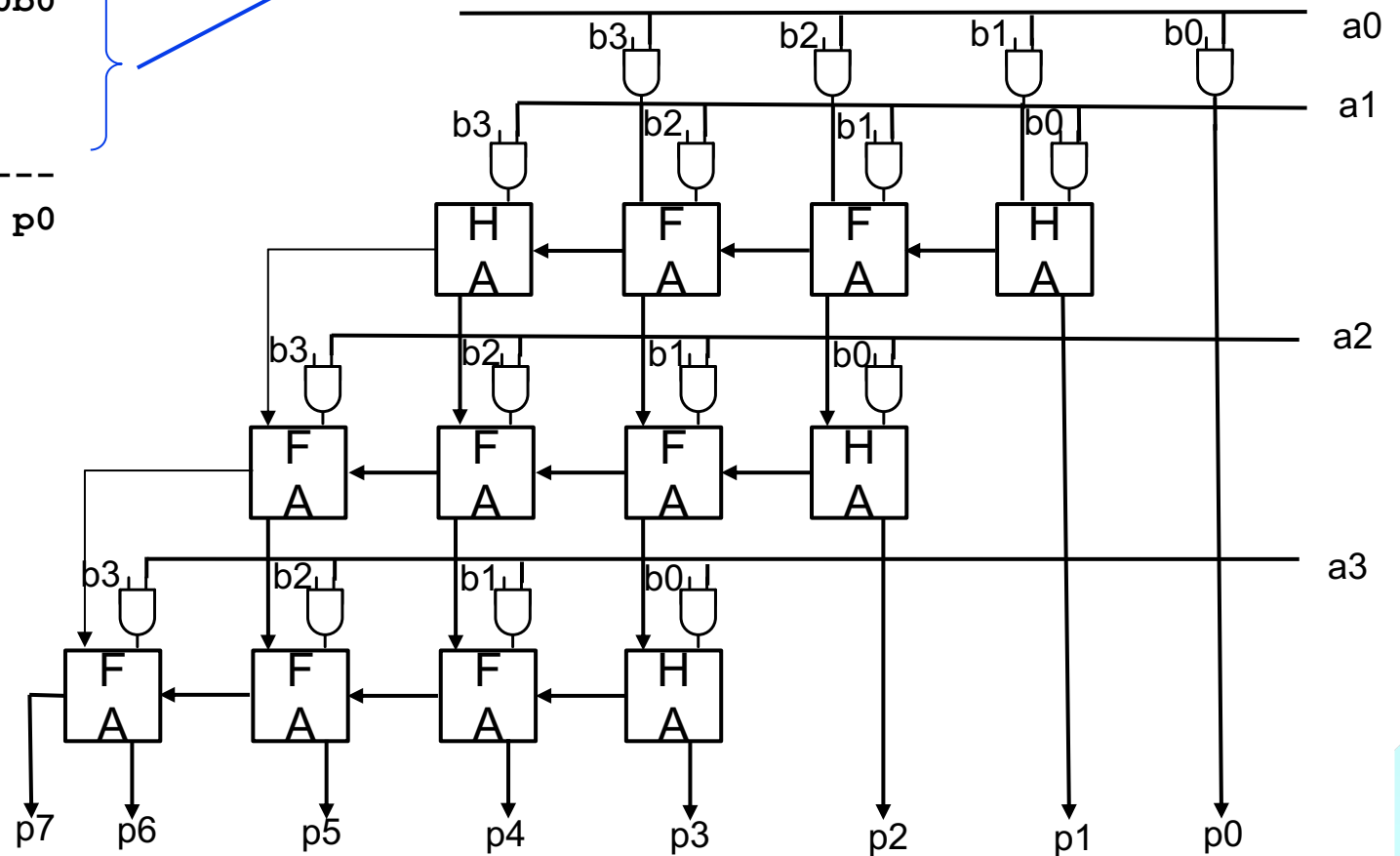
# Parallel (Array) Multiplier

$$\begin{array}{r}
 \begin{array}{cccc}
 & a3 & a2 & a1 & a0 \\
 * & b3 & b2 & b1 & b0 \\
 \hline
 & a3b0 & a2b0 & a1b0 & a0b0 \\
 + & & a3b1 & b2a1 & a1b1 & a0b1 \\
 + & & & a3b2 & a2b2 & a1b2 & a0b2 \\
 + & & & & a3b3 & a2b3 & a1b3 & a0b3 \\
 \hline
 p7 & p6 & p5 & p4 & p3 & p2 & p1 & p0
 \end{array}
 \end{array}$$

multiplicand multiplier  
 Partial products, one for each bit in multiplier  
 (each bit needs just one AND gate)




- Performance: What is the critical path?



 
# Parallel (Array) Multiplier

Single cycle multiply: Generates all  $n$  partial products simultaneously.



Each row:  $n$ -bit adder with AND gates

 

# Carry-Save Addition


- Speeding up multiplication is a matter of speeding up the summing of the partial products.
- “Carry-save” addition can help.
- Carry-save addition passes (saves) the carries to the output, rather than propagating them.

Example: sum three numbers,  
 $3_{10} = 0011$ ,  $2_{10} = 0010$ ,  $3_{10} = 0011$

$$\begin{array}{rcl}
 & 3_{10} & 0011 \\
 + & 2_{10} & 0010 \\
 \hline
 & c & 0100 = 4_{10} \\
 & s & 0001 = 1_{10}
 \end{array}
 \left. \vphantom{\begin{array}{rcl} & 3_{10} & 0011 \\ + & 2_{10} & 0010 \\ \hline & c & 0100 = 4_{10} \\ & s & 0001 = 1_{10} \end{array}} \right\} \text{carry-save add}$$
  


$$\begin{array}{rcl}
 & 3_{10} & 0011 \\
 + & & 0011 \\
 \hline
 & c & 0010 = 2_{10} \\
 & s & 0110 = 6_{10} \\
 & & 1000 = 8_{10}
 \end{array}
 \left. \vphantom{\begin{array}{rcl} & 3_{10} & 0011 \\ + & & 0011 \\ \hline & c & 0010 = 2_{10} \\ & s & 0110 = 6_{10} \\ & & 1000 = 8_{10} \end{array}} \right\} \begin{array}{l} \text{carry-save add} \\ \text{carry-propagate add} \end{array}$$

 - Carry-save addition takes in 3 numbers and produces 2: “3:2 compressor”
  - Whereas, carry-propagate takes 2 and produces 1.
- With this technique, we can avoid carry propagation until final addition



-
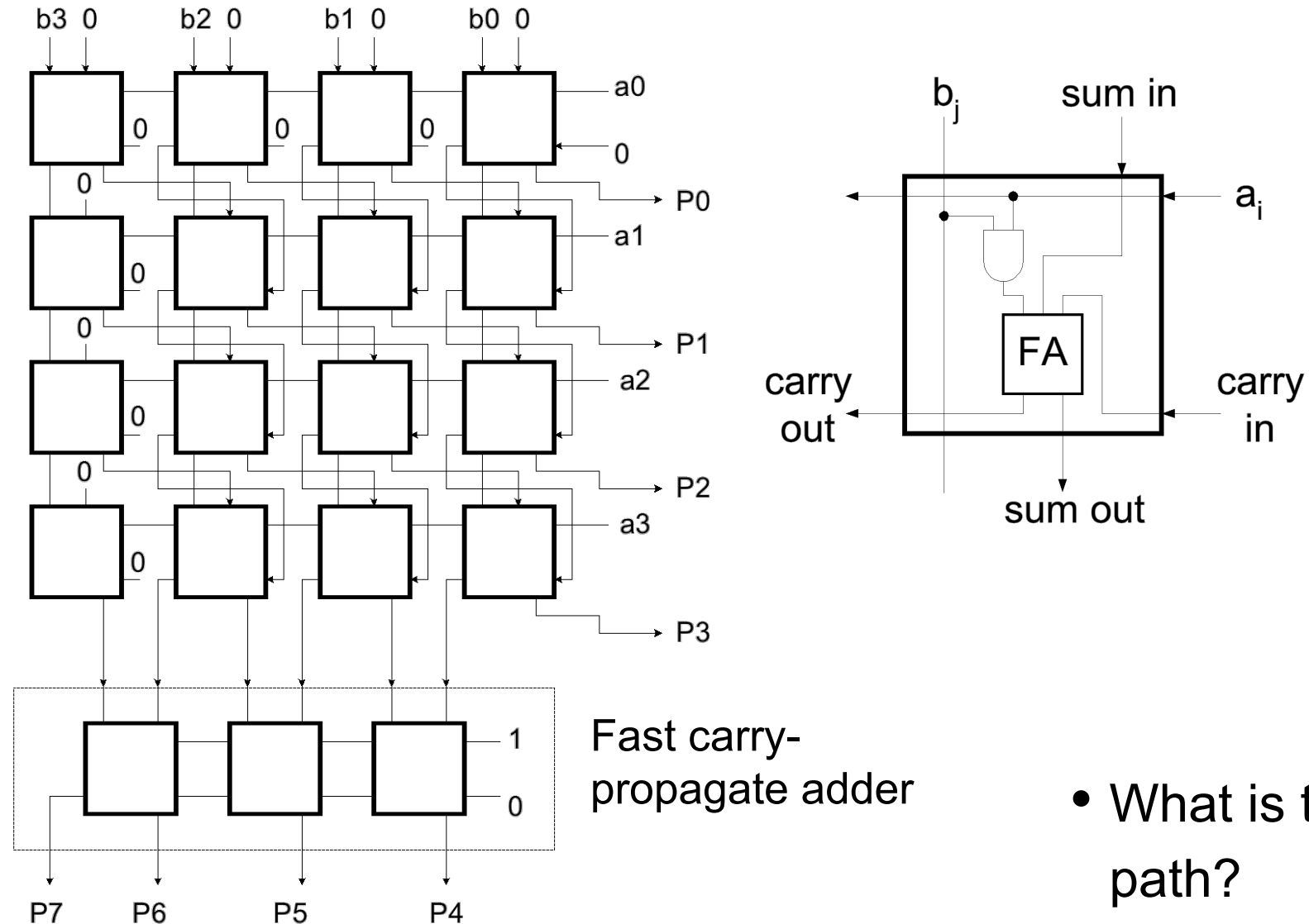
# Array Multiplier Using Carry-Save Addition




- What is the critical path?
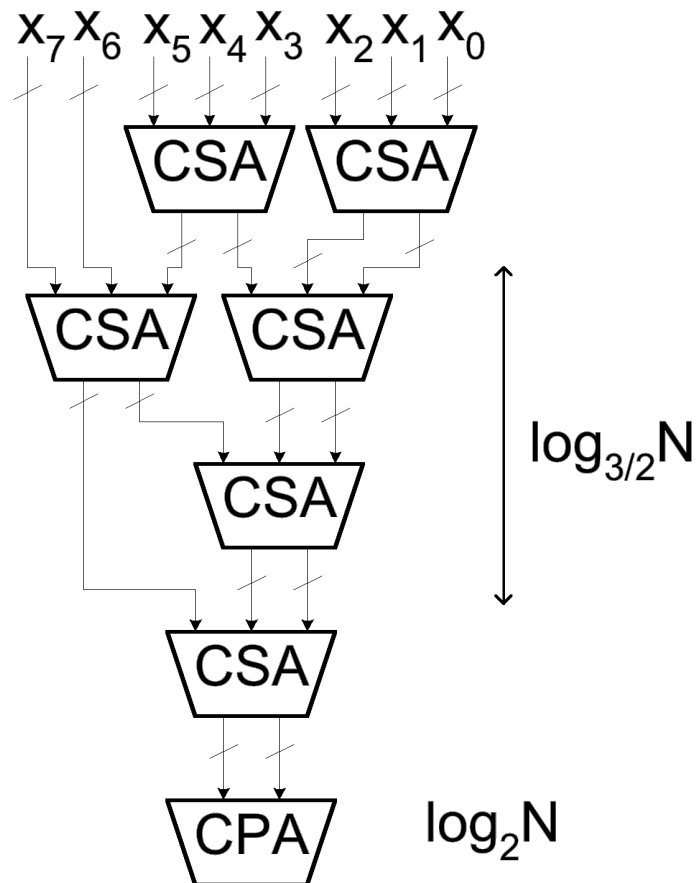
# Carry-Save Addition

CSA is associative and commutative. For example:

$$(((X_0 + X_1) + X_2) + X_3) = ((X_0 + X_1) + (X_2 + X_3))$$




- A balanced tree can be used to reduce the logic delay
- It doesn't matter where you add the carries and sums, as long as you eventually do add them
- This structure is the basis of the **Wallace Tree Multiplier**
- Partial products are summed with the CSA tree. Fast CPA (ex: CLA) is used for final sum
- Multiplier delay  $\propto \log_{3/2} N + \log_2 N$

# Wallace-Tree Multiplier


- Reduce the partial products in logic stages – 4 x 4 example

Partial products

 


(a)

First stage

 


(b)

Second stage

 


(c)

Final adder

 

(d)

# Wallace-Tree Multiplier

 


Note: Wallace tree is often slower than an array multiplier in FPGAs (which have optimized carry chains)


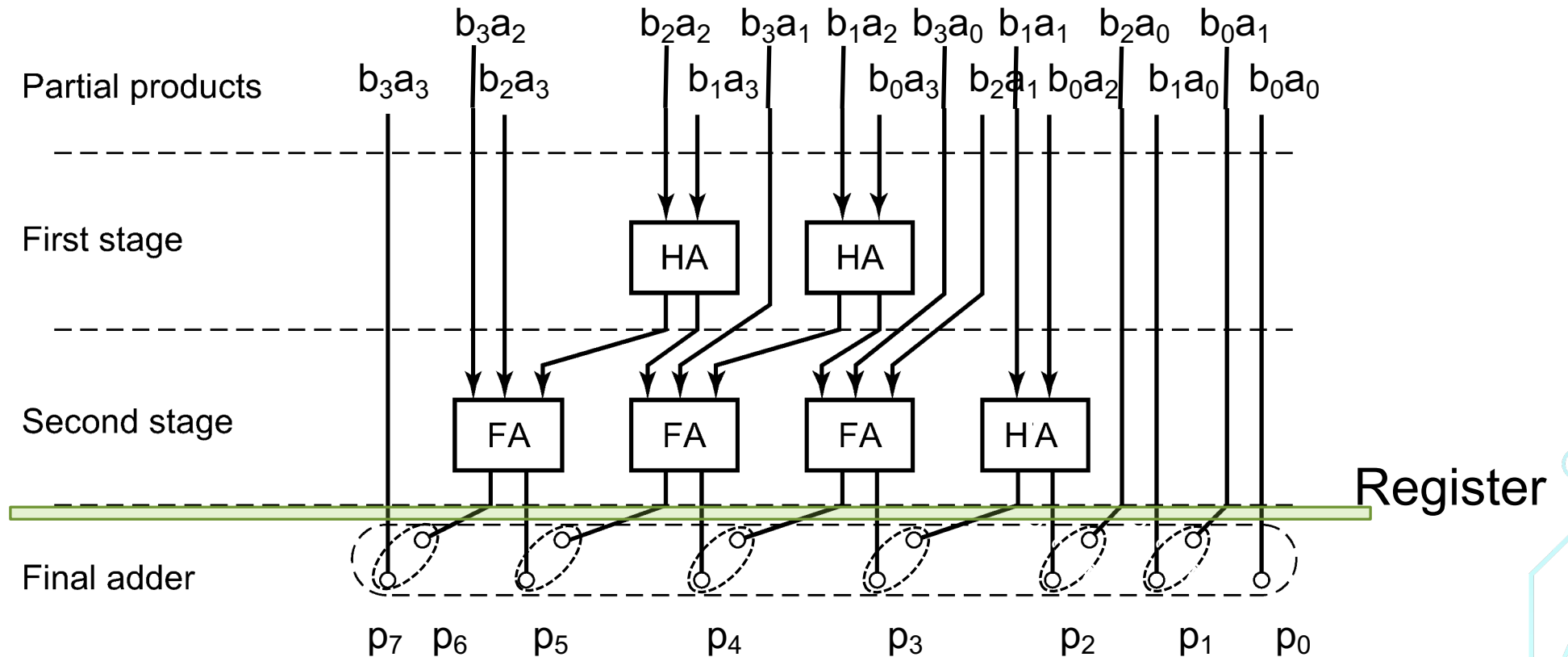
# Increasing Throughput: Pipelining

- Multipliers have a long critical path: PP generation  $\rightarrow$  reduction tree  $\rightarrow$  final adder
  - Often pipelined before final adder (2x flip-flops for carry-save)



# Administrivia

- New homework this week.
- Project, project, project!
  - Checkpoint 1 this week.



- **Multipliers**


- **Basics**
- **Parallel Multipliers**
- **Booth Recoding**
- **Signed Multipliers**


 
# Booth Recoding: Higher-radix multiplier

- Idea: If we could use, say, 2 bits of the multiplier in generating each partial product we would **halve the number of columns and speed it up!**
- Encode ...0111100... patterns:
  - $1111 = 2^3 + 2^2 + 2^1 + 2^0 = 2^4 - 2^0$
  - Only two non-zero numbers, but needs to represent +1 and -1

Booth's insight:  
rewrite  $2 \cdot A$  and  $3 \cdot A$   
cases, leave  $4A$  for  
next partial product  
to do!



$$\begin{aligned}
 B_{K+1,K} \cdot A &= 0 \cdot A \rightarrow 0 \\
 &= 1 \cdot A \rightarrow A \\
 &= 2 \cdot A \rightarrow 2A \text{ (or } 4A - 2A) \\
 &= 3 \cdot A \rightarrow 4A - A
 \end{aligned}$$

# Booth recoding

(On-the-fly canonical signed digit encoding!)

current bit pair

from previous bit pair

$B_{K+1}$	$B_K$	$B_{K-1}$	action
0	0	0	add 0
0	0	1	add A
0	1	0	add A
0	1	1	add 2*A
1	0	0	sub 2*A
1	0	1	sub A
1	1	0	sub A
1	1	1	add 0


$$\begin{aligned} B_{K+1,K} * A &= 0 * A \rightarrow 0 \\ &= 1 * A \rightarrow A \\ &= 2 * A \rightarrow 4A - 2A \\ &= 3 * A \rightarrow 4A - A \end{aligned}$$

$$\leftarrow -2 * A + A$$

# Example

- Compression tree needs to support subtraction

	0111	A
x	1010	B
-----		
	-01110	10 (0) -2A
	-00111	101 -A
	+0111	001 +A
-----		
	01000110	

 

A Walther WSR160 arithmometer  
(from Wikipedia)



# Booth Recoding Notes

- Key advantage: Reduces the number of partial products
  - Compression tree depth becomes  $\log_{3/2}[N/2]$
  - Partial product generation is slightly more complex than a NAND2
- Useful for larger multipliers
  - And some very creative solutions for repeated multiplications (FIR filters, etc)



- **Multipliers**

- **Basics**
- **Parallel Multipliers**
- **Booth Recoding**
- **Signed Multipliers**

# “Shift and Add” Multiplier

## Signed Multiplication:

*Remember for 2's complement numbers MSB has negative weight:*


$$X = \sum_{i=0}^{N-2} x_i 2^i - x_{n-1} 2^{n-1}$$

$$\begin{aligned} \text{ex: } -6 &= 11010_2 = 0 \cdot 2^0 + 1 \cdot 2^1 + 0 \cdot 2^2 + 1 \cdot 2^3 - 1 \cdot 2^4 \\ &= 0 + 2 + 0 + 8 - 16 = -6 \end{aligned}$$

- Therefore for multiplication:
  - a) subtract final partial product
  - b) sign-extend partial products

# Signed Array Multiplier

- Two's complement

 

**(-3)**  
**(-2)**

**1** 0 1 (X)  
\* **1** 1 0 (Y)

0 0 0 0 0 0  
+ **1** **1** 1 0 1  
- **1** 1 0 1

$Y_0 * X = 0$   
 $2Y_1 * X = -6$   
 $4Y_2 * X = -12$

**(+6)**

0 0 0 1 1 0



# Convince yourself

- What's  $-3 \times 5$ ?

$$\begin{array}{r} 1101 \\ \times 0101 \\ \hline \end{array}$$
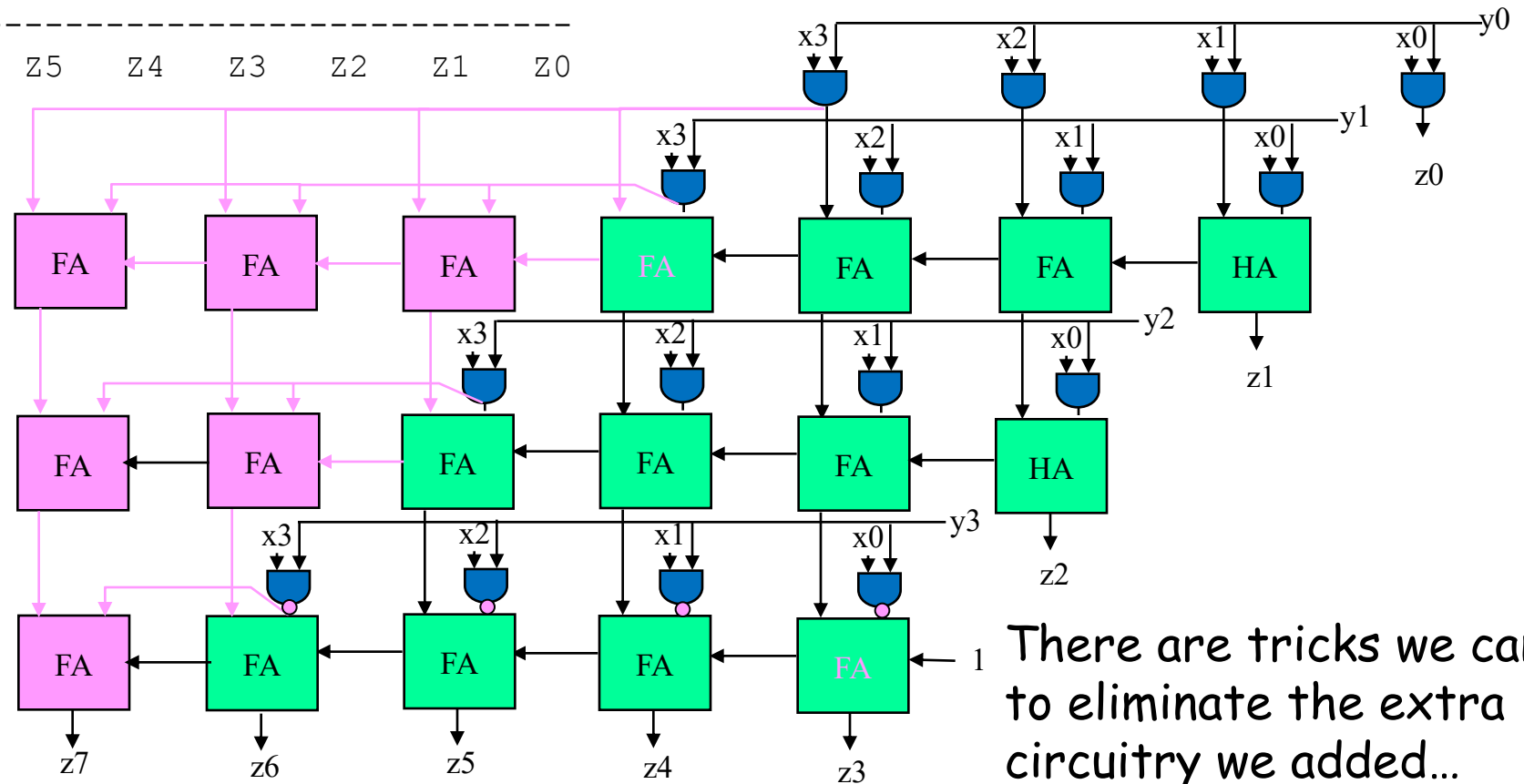 
# Combinational Multiplier (signed)

$$\begin{array}{r}
 \begin{array}{cccc}
 & X3 & X2 & X1 & X0 \\
 * & Y3 & Y2 & Y1 & Y0 \\
 \hline
 & X3Y0 & X3Y0 & X3Y0 & X3Y0 & X2Y0 & X1Y0 & X0Y0 \\
 + & X3Y1 & X3Y1 & X3Y1 & X3Y1 & X2Y1 & X1Y1 & X0Y1 \\
 + & X3Y2 & X3Y2 & X3Y2 & X2Y2 & X1Y2 & X0Y2 & \\
 - & X3Y3 & X3Y3 & X2Y3 & X1Y3 & X0Y3 & & \\
 \hline
 & Z7 & Z6 & Z5 & Z4 & Z3 & Z2 & Z1 & Z0
 \end{array}
 \end{array}$$



There are tricks we can use to eliminate the extra circuitry we added...

# 2's Complement Multiplication (Baugh-Wooley)

Step 1: two's complement operands so high order bit is  $-2^{N-1}$ . Must sign extend partial products and **subtract** the last one

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & \textcolor{red}{x3} & x2 & x1 & x0 \\
 * & & & & \textcolor{red}{y3} & y2 & y1 & y0 \\
 \hline
 & & & & & & & & \\
 \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & x2y2 & x1y2 & x0y2 & \\
 - & \textcolor{red}{x3y3} & \textcolor{red}{x3y3} & x2y3 & x1y3 & x0y3 & & \\
 \hline
 & z7 & z6 & z5 & z4 & z3 & z2 & z1 & z0
 \end{array}
 \end{array}$$

Step 2: don't want all those extra additions, so add a carefully chosen constant, remembering to subtract it at the end. Convert subtraction into add of (complement + 1).

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & & & & & & & & \textcolor{red}{1} \\
 + & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & & & & & & & & \textcolor{red}{1} \\
 + & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & x2y2 & x1y2 & x0y2 & \\
 + & & & & & & & & \textcolor{red}{1} \\
 + & \textcolor{red}{x3y3} & \textcolor{red}{x3y3} & \textcolor{red}{x2y3} & \textcolor{red}{x1y3} & \textcolor{red}{x0y3} & & & \textcolor{red}{1} \\
 + & & & & & & & & \textcolor{red}{1} \\
 + & & & & & & & & \textcolor{red}{1} \\
 - & & & & & & & & \textcolor{red}{1}
 \end{array}
 \end{array}
 \left. \vphantom{\begin{array}{r} \textcolor{red}{x3y3} \textcolor{red}{x3y3} \textcolor{red}{x2y3} \textcolor{red}{x1y3} \textcolor{red}{x0y3} \end{array}} \right\} -B = \sim B + 1$$

Step 3: add the ones to the partial products and propagate the carries. All the sign extension bits go away!

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & & & & & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & & & & & & & & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & & & & \textcolor{red}{x2y2} & x1y2 & x0y2 & & & & & \\
 + & & \textcolor{red}{x3y3} & x2y3 & x1y3 & x0y3 & & & & & & \\
 + & & & & & & & & & & & 1 \\
 - & & & 1 & 1 & 1 & 1 & & & & & 1
 \end{array}
 \end{array}$$


Step 4: finish computing the constants...

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & & & & & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & & & & & & & & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & & & & \textcolor{red}{x2y2} & x1y2 & x0y2 & & & & & \\
 + & & \textcolor{red}{x3y3} & x2y3 & x1y3 & x0y3 & & & & & & \\
 + & & & & & & & & & & & 1 \\
 + & 1 & & & & & & & & & & 1
 \end{array}
 \end{array}$$

Result: multiplying 2's complement operands takes just about same amount of hardware as multiplying unsigned operands!


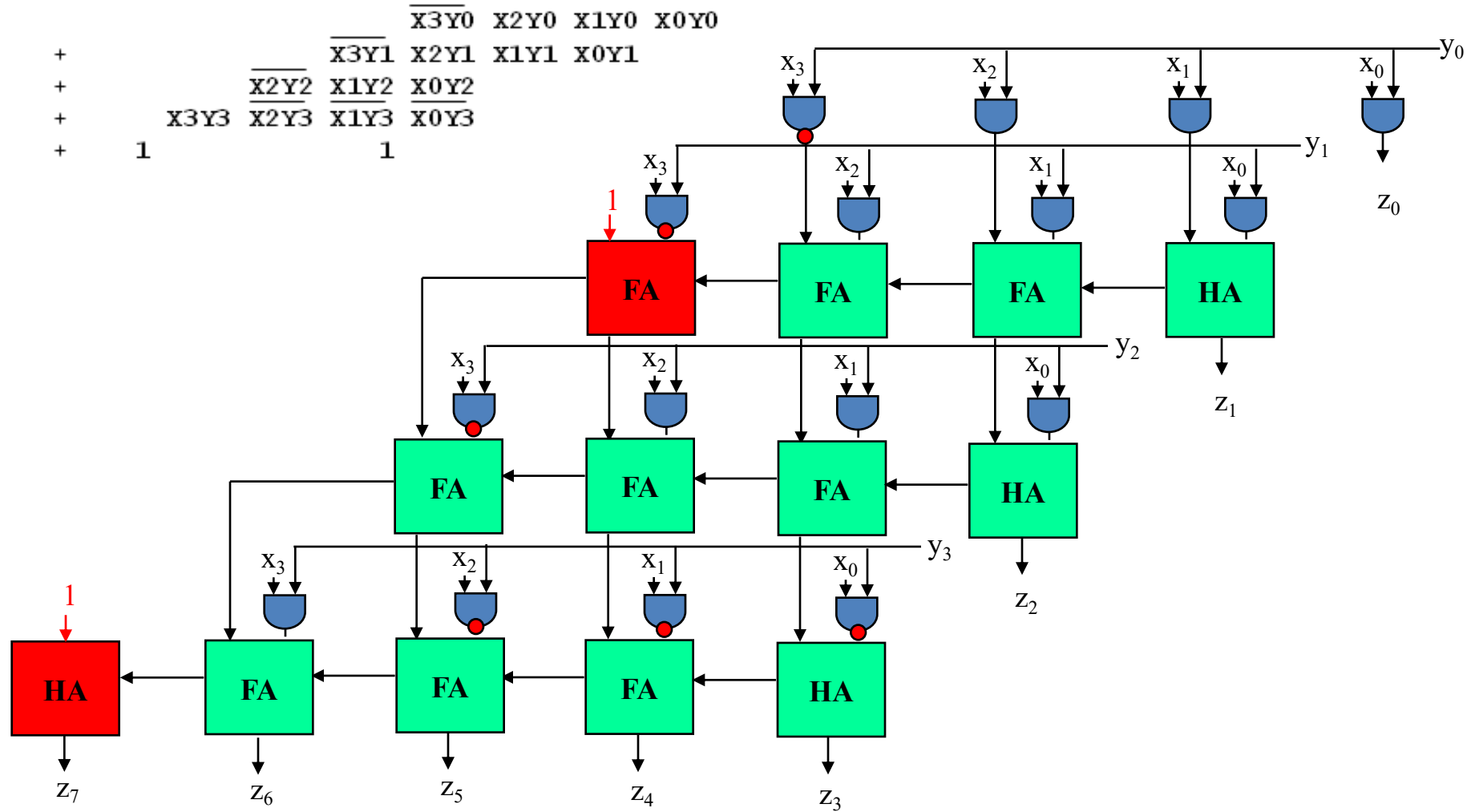
# 2's Complement Multiplication (Baugh-Wooley)



# Summary

- Binary number multiplications
  - Shift-and-add multiplier
- Parallel adder array
- Partial-Product accumulation
  - Carry-save adder
  - Wallace Tree multiplier
- Partial-Product Generation
  - Booth Encoding