

# EECS151/251A

## Introduction to Digital Design and ICs


### Lecture 19: Energy & Adders

Sophia Shao



 **ACM TURING AWARD HONORS JACK J. DONGARRA FOR PIONEERING CONCEPTS AND METHODS WHICH HAVE RESULTED IN WORLD-CHANGING COMPUTATIONS**

Dongarra's Algorithms and Software Fueled the Growth of High-Performance Computing and Had Significant Impacts in Many Areas of Computational Science from AI to Computer Graphics



# Summary

- Wire also contributes to delay, especially in modern technology.
- We can use RC model to capture wire delay as well.
- Energy becomes an increasingly important optimization goal.
  - Dynamic Energy
  - Static Energy





- **Energy**
  - Overview
  - Dynamic & Static
- **Adders**
  - Single-Bit Full Adder
  - Ripple-Carry Adder
  - Carry-Bypass Adder
  - Carry-Lookahead Adder

# Where does power go in CMOS?

- Dynamic Power Consumption
  - Charging and discharging capacitors
  - Short-Circuit Currents
    - Short-circuit path between supply rails during switching
- Leakage (Static) Power
  - Leaky transistors

  
# #1: Dynamic Power Consumption

- Voltage and frequency scaling (lower  $V_{dd}$ ,  $f$ )





$$Power = \alpha * C_L * V_{dd}^2 * f_{clk}$$

 - Reduce capacitance (lower  $C_L$ )
  - Gate: minimize device sizes w/o significantly hurting perf.
  - Wire: shorten long wires
- Reduce activity factor (lower  $\alpha$ )
  - Clock gating





## #2: Short-circuit Current

- During transition, both PUD and PDN are on.
- Similar to dynamic power, related to switching activity.
- Typically small, <10% of total power consumption
- Becomes less important in advanced technology
  - Threshold voltages do not scale as fast as supply voltage.
  - If  $V_{dd} < V_{thn} + |V_{thp}|$ , no short circuit.

  
 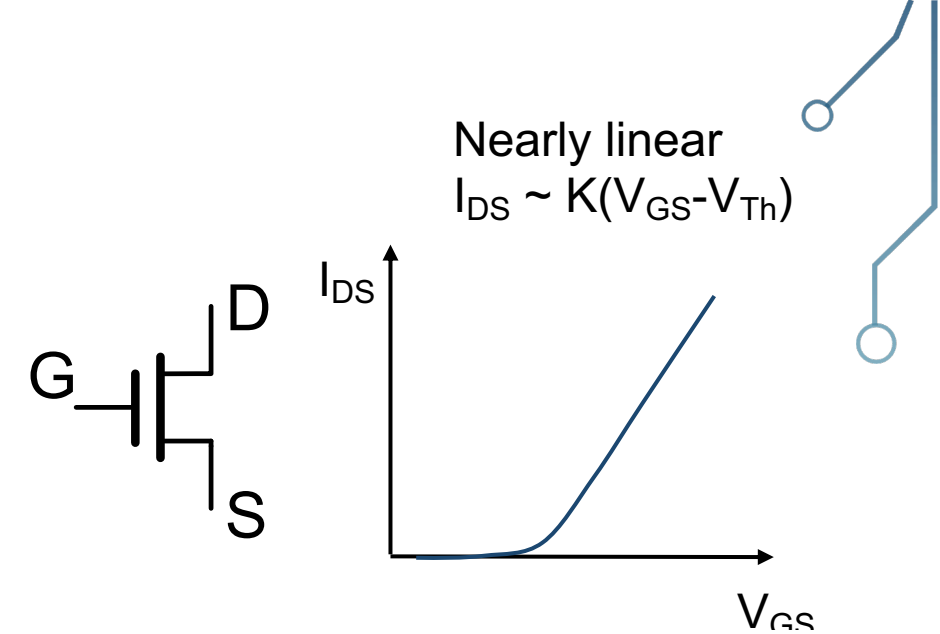
# #3 Leakage (Static) Power

- Power is consumed with a chip is not switching.
  - “Off” is not really off.
- Subthreshold leakage currents grow exponentially with increases in temperature and decreases in threshold voltage.
  - But threshold voltage scaling is key to circuit performance.
- To reduce leakage power
  - Power gating: Turn OFF power to blocks when they are idle to save leakage
  - Use high-Vt cells.



$I_{DS}$  Vs  $V_{GS}$  characteristics in log scale






- **Energy**
  - Overview
  - Dynamic & Static
- **Adders**
  - **Single-Bit Full Adder**
  - **Carry-Ripple Adder**
  - **Carry-Bypass Adder**
  - **Carry-Lookahead Adder**


 
# Binary Adder

- Adders

```
module add32(i0,i1,sum);  
input  [31:0] i0,i1;  
output [31:0] sum;  
  
assign sum = i0 + i1;  
endmodule
```




What's inside?

Depends on:

- Performance/power requirements
- Number of bits

# Single-Bit Full-Adder

 

$$S = A \bar{B} \bar{C}_i + \bar{A} B \bar{C}_i + \bar{A} \bar{B} C_i + A B C_i$$

$$S = A \oplus B \oplus C_i$$

$$C_o = A B + B C_i + A C_i$$

A	B	C <sub>in</sub>	C <sub>o</sub>	S
0	0	0	0	0
		1	0	1
0	1	0	0	1
		1	1	0
1	0	0	0	1
		1	1	0
1	1	0	1	0
		1	1	1

		ab			
		00	01	11	10
c	0	0	0	1	0
	1	0	1	1	1


$$\text{cout} = ab + bc + ac$$

# Static CMOS Full Adder

- Direct mapping of logic equations

$$C_o = A B + B C_i + A C_i$$
$$\overline{C_o} = \overline{AB + C_i(A + B)}$$
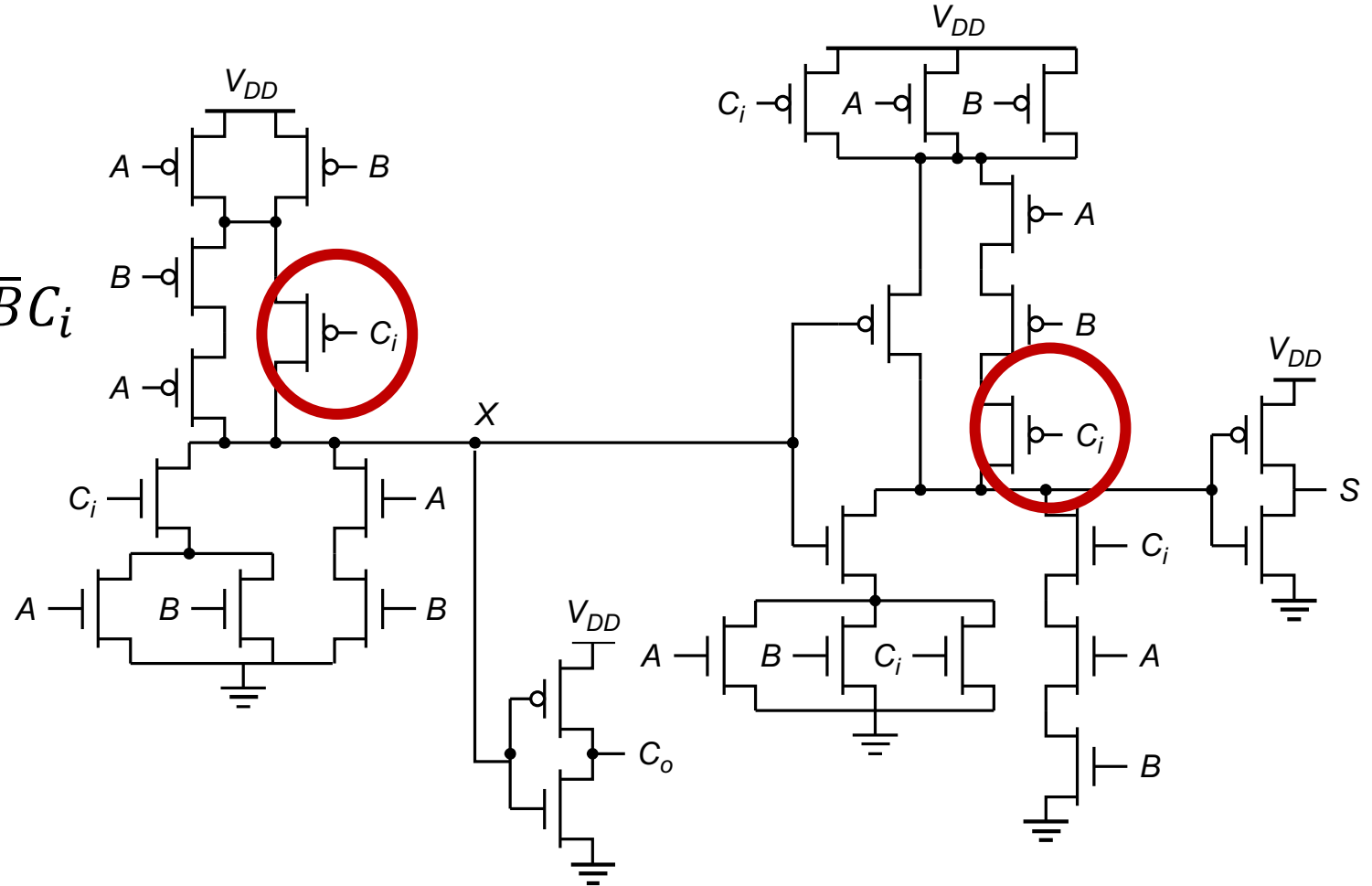
$$S = ABC_i + A\overline{B}\overline{C_i} + \overline{A}B\overline{C_i} + \overline{A}\overline{B}C_i$$
$$= ABC_i + (A + B + C_i) \overline{C_o}$$



28 Transistors

# Express Sum and Carry as a function of P, G, D

- Define generate, propagate and kill as functions of inputs
  - Will use two at a time

**Generate (G) = AB**

**Propagate (P) =  $A \oplus B$ , close to (A+B)**

**Kill (K) =  $\bar{A} \bar{B}$**

$$C_o = A B + B C_i + A C_i = G + P C_i$$

$$S = P \oplus C_i$$

A	B	C <sub>in</sub>	G	P	K	C <sub>o</sub>	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

Can also derive expressions for C<sub>o</sub> based on K and P

# Why Generate and Propagate?

- Ripple-carry adders have to wait for the carry of each bit pair to be computed before getting the result.
  - This can take a long time!
- G and P depend only on A and B, not on C (the carry)
  - Thus, we can compute G and P for all bits in parallel
  - Then, the idea is that we can more easily compute the sum without having to wait for carries

**Generate (G) =  $AB$**

**Propagate (P) =  $A \oplus B$ , close to  $(A+B)$**

# Announcement

- Project starts!
  - Checkpoint 1 this week.
  - Wrap up your labs if you haven't done so already.
- Homework 7 out this week.




- Energy
  - Overview
  - Dynamic & Static
- Adders
  - Single-Bit Full Adder
  - **Carry-Ripple Adder**
  - **Carry-Bypass Adder**
  - **Carry-Lookahead Adder**



# The Ripple-Carry Adder

- 4-bit adder

 


**Worst case delay linear with the number of bits**

$$t_d = O(N)$$

$$t_{\text{adder}} = (N-1)t_{\text{carry}} + t_{\text{sum}}$$

Goal: Make the fastest possible carry path circuit


# Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$
 
# Minimize Critical Path by Reducing Inverting Stages




**Exploit Inversion Property**



- Energy
  - Overview
  - Dynamic & Static
- Adders
  - Single-Bit Full Adder
  - Carry-Ripple Adder
  - **Carry-Bypass Adder**
  - **Carry-Lookahead Adder**


# Carry-Bypass Adder

- Also called 'carry skip'

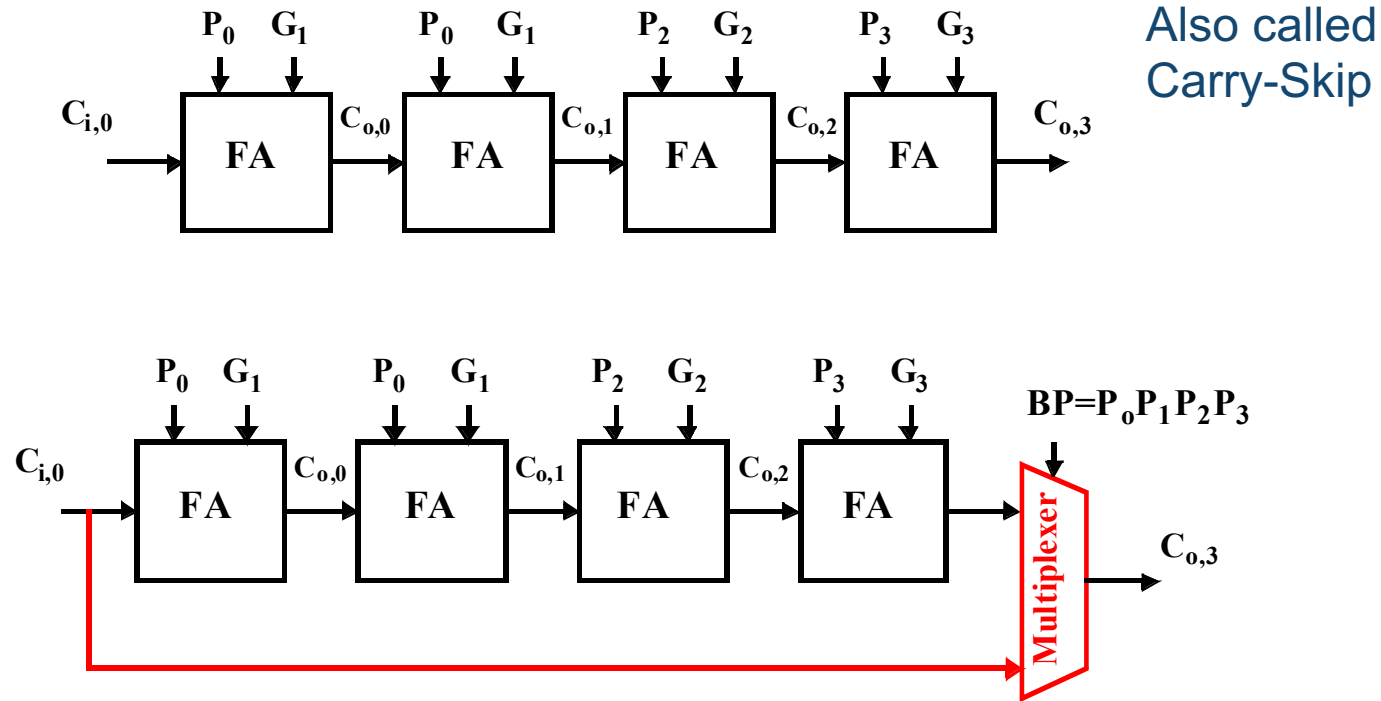


Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ )  
then  $C_{o3} = C_0$ , else “kill” or “generate”.

# Carry-Bypass Adder (cont.)

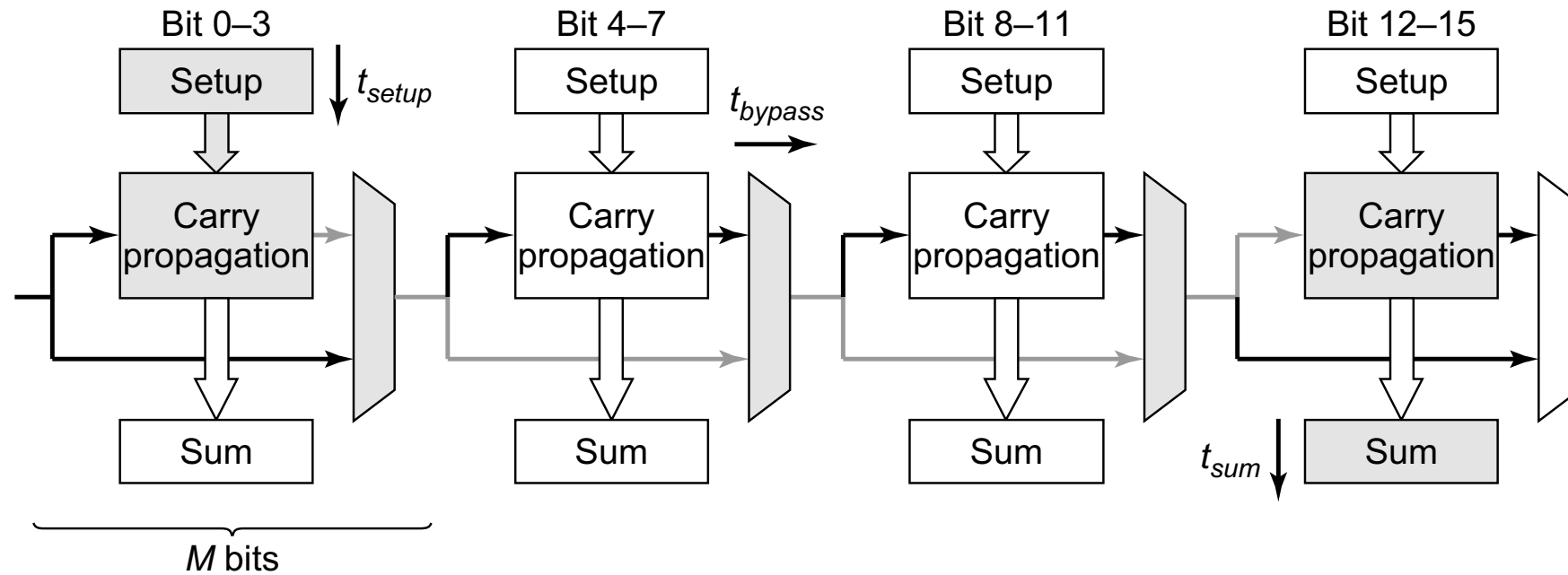

$$t_{adder} = t_{setup} + (M-1) t_{carry} + (N/M-1)t_{bypass} + (M-1)t_{carry} + t_{sum}$$

# Carry Ripple versus Carry Bypass

 


- Depends on technology, design constraints






- Energy
  - Overview
  - Dynamic & Static
- Adders
  - Single-Bit Full Adder
  - Carry-Ripple Adder
  - Carry-Bypass Adder
  - **Carry-Lookahead Adder**

# Trees for optimization

 

$T = O(N)$
 
$$((((((x_0 + x_1) + x_2) + x_3) + x_4) + x_5) + x_6) + x_7$$




$T = O(\log N)$

$$((x_0 + x_1) + (x_2 + x_3)) + ((x_4 + x_5) + (x_6 + x_7))$$

- “+” is associative.
 
# Parallel Prefix, or “Scan”

- If “+” is an associative operator, and  $x_0, \dots, x_{p-1}$  are input data then *parallel prefix* operation computes:  $y_j = x_0 + x_1 + \dots + x_j$  for  $j=0,1,\dots,p-1$




# Lookahead - Basic Idea

**Generate (G) = AB**

**Propagate (P) =  $A \oplus B$ , close to  $(A+B)$**

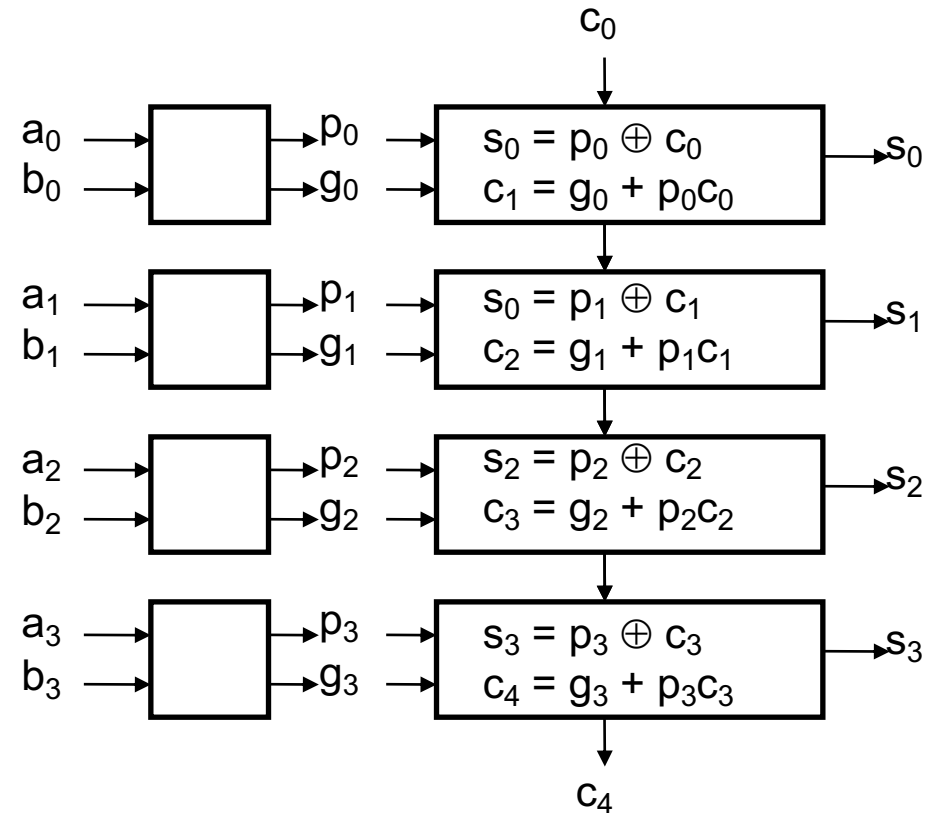**Kill (K) =  $\bar{A} \bar{B}$**

$$C_o = A B + B C_i + A C_i = G + P C_i$$



- So far, no advantage over ripple adder:  $T \propto N$

# Lookahead - Basic Idea

Expanding lookahead equations:

$$C_{o,1} = G_1 + P_1 C_{i,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

Carry at bit k:


$$C_{o,k} = G_k + P_k (G_{k-1} + P_{k-1} C_{o,k-2})$$

Expanding at bit k:

$$C_{o,k} = G_k + P_k (G_{k-1} + P_{k-1} (\dots + P_1 (G_0 + P_0 C_{i,0}) \dots))$$


Carry-lookahead gate grows at each bit position!
 
$$C_o = A B + B C_i + A C_i = G + P C_i$$



 
# Lookahead - Basic Idea

- “Group” propagate and generate signals:
- P true if the group as a whole propagates a carry to  $c_{out}$
- G true if the group as a whole generates a carry
- Group P and G can be generated hierarchically



$$c_{out} = G + P c_{in}$$


# Carry Look-ahead Adders

 

$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$



# Carry Look-ahead Adders

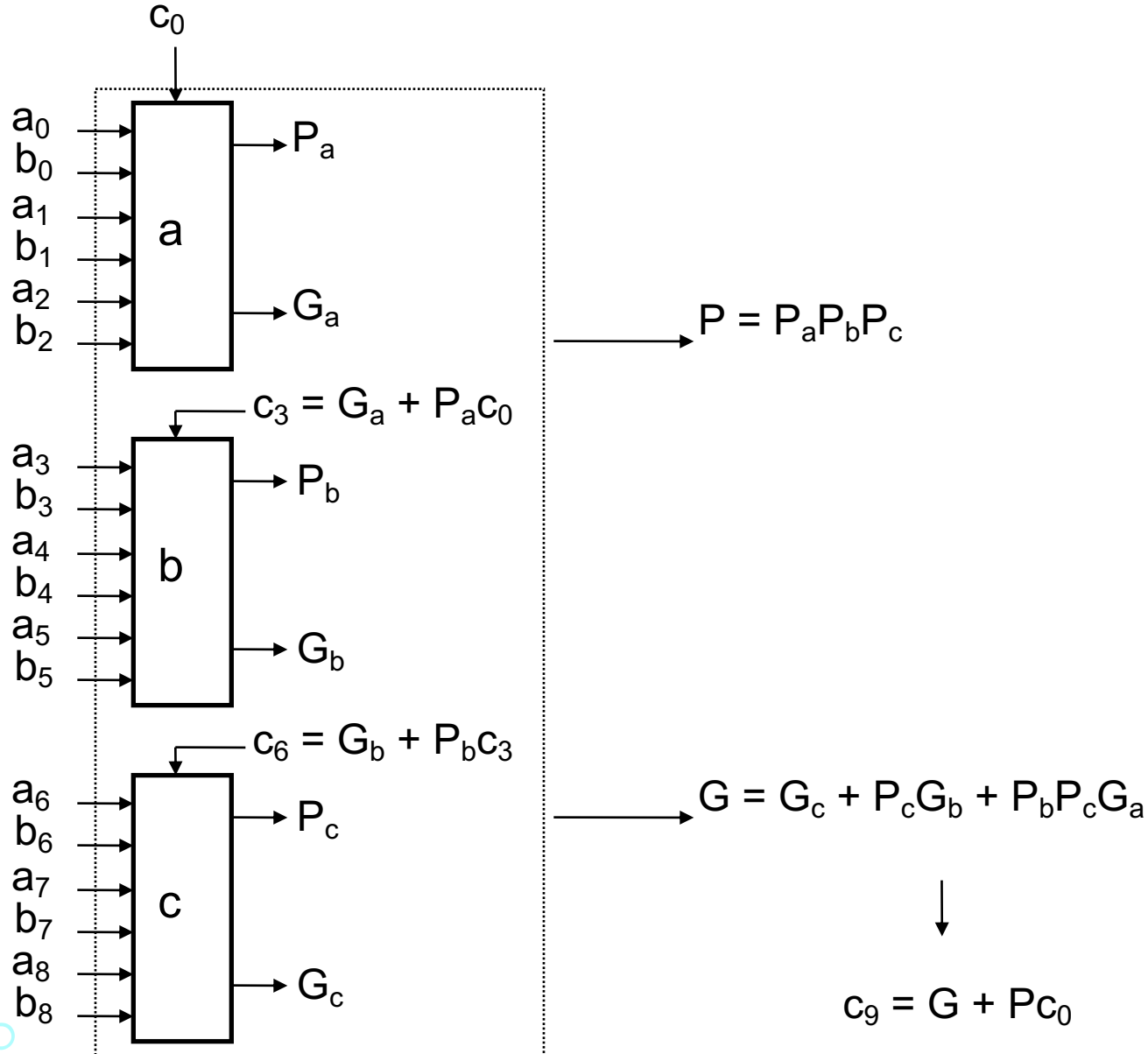

9-bit Example of hierarchically generated P and G signals:

# Carry Lookahead Trees

Build the carry-lookahead tree as a hierarchy of gates

$$C_{o,0} = G_0 + P_0 C_{i,0}$$

$$C_{o,1} = G_1 + P_1 C_{i,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$\begin{aligned} C_{o,2} &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0} \\ &= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{o,0} \end{aligned}$$

Can continue building the tree hierarchically.

# Logarithmic (Tree) Adders – Idea


- “Look ahead” across groups of multiple bits to figure out the carry

- Example with two-bit groups:

$$P_{1:0} = P_1 \cdot P_0, G_{1:0} = G_1 + P_1 \cdot G_0, \rightarrow C_{\text{out}1} = G_{1:0} + P_{1:0} \cdot C_{0,\text{in}}$$

- Combine these groups in a tree structure:


- Delay is now  $\sim \log_2(N)$

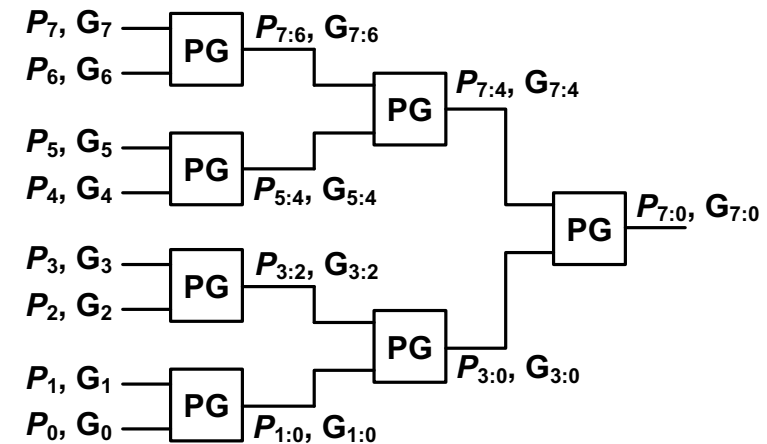

# Many Kinds of Tree Adders


- ❑ Many ways to construct these tree (or “carry lookahead”) adders
  - Many of these variations named after the people who first came up with them
- ❑ Most of these vary three basic parameters:
  - Radix: how many bits are combined in each PG gate
    - Previous example was radix 2; often go up to radix 4
  - Tree depth: stages of logic to the final carry. Must be at least  $\log_{\text{Radix}}(N)$
  - Sparseness

# Tree Adders

 


**16-bit radix-2 Kogge-Stone tree**

# Tree Adders

 

**16-bit radix-4 Kogge-Stone Tree**


# Sparse Trees

 

**16-bit radix-2 sparse tree with sparseness of 2**



# Tree Adders

 

**Brent-Kung Tree**

# Summary

- Binary adders are a common building block of digital systems
- Carry is in the critical path
- Carry-bypass is usually faster than ripple-carry for lengths  $> 8$
- Carry-lookahead,  $O(\sim \log N)$  is often the fastest adder with  $N > 16$